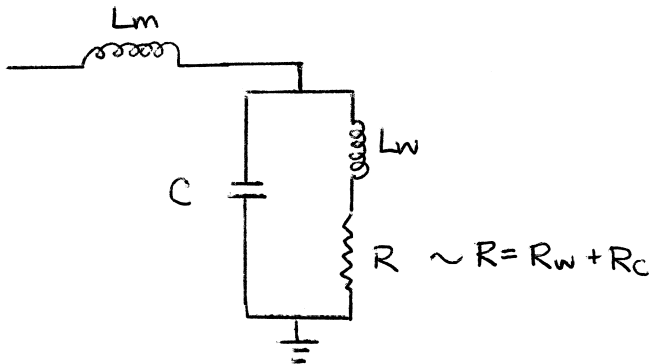


Resonant Tank Circuit



$$\begin{aligned}
 Z_{\text{total}} &= j\omega L_m + \frac{1}{j\omega C} \parallel (j\omega L_w + R) \\
 &= j\omega L_m + \frac{\frac{1}{j\omega C} (R + j\omega L_w)}{\frac{1}{j\omega C} + R + j\omega L_w} \times \frac{j\omega C}{j\omega C} \\
 &= j\omega L_m + \frac{R + j\omega L_w}{1 + R(j\omega C) - \omega^2 C L_w} \times \frac{(1 - \omega^2 C L_w) - j\omega C R}{(1 - \omega^2 C L_w) - j\omega C R} \\
 &= j\omega L_m + \frac{R(1 - \omega^2 C L_w) - j\omega C R^2 + j\omega L_w(1 - \omega^2 C L_w) + \omega^2 C R L_w}{(1 - \omega^2 C L_w)^2 + (\omega C R)^2} \\
 &= j\omega L_m + \frac{R - \omega^2 C R L_w - j\omega C R^2 + j\omega L_w - j\omega^3 C L_w^2 + \omega^2 C R L_w}{(1 - \omega^2 C L_w)^2 + (\omega C R)^2} \\
 &= \frac{j\omega L_m [(1 - \omega^2 C L_w)^2 + (\omega C R)^2] + (R - \omega^2 C R L_w + \omega^2 C R L_w) + j(\omega L_w - \omega^3 C L_w^2 - \omega C R^2)}{(1 - \omega^2 C L_w)^2 + (\omega C R)^2} \\
 &= \frac{j\omega L_m [(1 - 2\omega^2 C L_w + \omega^4 C^2 L_w^2) + \omega^2 C^2 R^2] + R + j(\omega L_w - \omega^3 C L_w^2 - \omega C R^2)}{(1 - \omega^2 C L_w)^2 + (\omega C R)^2} \\
 &= \frac{(R + \omega^2 C^2 R^2) + j[\omega L_m - 2\omega^3 C L_m L_w + \omega^5 C^2 L_m L_w^2 + \omega^3 C^2 R^2 L_m + \omega L_w - \omega^3 C L_w^2 - \omega C R^2]}{(1 - \omega^2 C L_w)^2 + (\omega C R)^2}
 \end{aligned}$$

set the imaginary part to zero:

$$\omega L_m - 2\omega^3 C L_m L_w + \omega^5 C^2 L_m L_w^2 + \omega^3 C^2 R^2 L_m + \omega L_w - \omega^3 C L_w^2 - \omega C R^2 = 0$$

$$\omega^5 C^2 L_m L_w^2 + \omega^3 (C^2 R^2 L_m - C L_w^2 - 2C L_m L_w) + \omega (L_m + L_w - C R^2) = 0$$

$$\omega [\omega^4 C^2 L_m L_w^2 + \omega^2 (L_m C^2 R^2 - C L_w^2 - 2 C L_m L_w) + (L_m + L_w - C R^2)] = 0$$

$$\omega = 0 \quad \text{OR}$$

$$\omega^2 = \frac{-(L_m C^2 R^2 - C L_w^2 - 2 C L_m L_w) \pm \sqrt{(L_m C^2 R^2 - C L_w^2 - 2 C L_m L_w)^2 - 4 C^2 L_m L_w^2 (L_m + L_w - C R^2)}}{2 L_m C^2 L_w^2} \quad \text{②}$$

Note:

$$\begin{aligned} \text{① } (L_m C^2 R^2 - C L_w^2 - 2 C L_m L_w)^2 &= L_m^2 C^4 R^4 - C^3 R^2 L_m L_w^2 - 2 C^3 R^2 L_m^2 L_w - C^3 R^2 L_m L_w^2 + C^2 L_w^4 + 2 C^2 L_m L_w^3 - 2 C^3 R^2 L_m^2 L_w \\ &\quad + 2 C^2 L_m L_w^3 + 4 C^2 L_m^2 L_w^2 \\ &= C^2 L_w^4 + 4 C^2 L_m L_w^3 + 4 C^2 L_m^2 L_w^2 - C^3 R^2 L_m L_w^2 - 4 C^3 R^2 L_m^2 L_w - C^3 R^2 L_m L_w^2 + C^4 R^4 L_m^2 \\ &= C^2 L_w^4 + 4 C^2 L_m L_w^3 + 4 C^2 L_m^2 L_w^2 - 2 C^3 R^2 L_m L_w^2 - 4 C^3 R^2 L_m^2 L_w + C^4 R^4 L_m^2 \end{aligned}$$

$$\text{①} + \text{②} = C^2 L_w^4 + 4 C^2 L_m L_w^3 + 4 C^2 L_m^2 L_w^2 - 2 C^3 R^2 L_m L_w^2 - 4 C^3 R^2 L_m^2 L_w + C^4 R^4 L_m^2 - 4 C^2 L_m^2 L_w^2 - 4 C^2 L_m L_w^3 + 4 C^3 R^2 L_m L_w^2$$

$$= C^2 L_w^4 + 2 C^3 R^2 L_m L_w^2 - 4 C^3 R^2 L_m^2 L_w + C^4 R^4 L_m^2$$

$$\omega^2 = -\frac{L_m C^2 R^2}{2 C^2 L_m L_w^2} + \frac{C L_w^2}{2 C^2 L_m L_w^2} + \frac{2 C L_m L_w}{2 C^2 L_m L_w^2} \pm \sqrt{\frac{C^2 L_w^4}{4 C^4 L_m^2 L_w^4} + \frac{2 C^3 R^2 L_m L_w^2}{4 C^4 L_m^2 L_w^4} + \frac{-4 C^3 R^2 L_m^2 L_w + C^4 R^4 L_m^2}{4 C^4 L_m^2 L_w^4}}$$

$$= -\frac{R^2}{2 L_w^2} + \frac{1}{2 C L_m} + \frac{1}{C L_w} \pm \sqrt{\frac{1}{4 C^2 L_m^2} + \frac{R^2}{2 C L_m L_w^2} - \frac{R^2}{C L_w^3} + \frac{R^4}{4 L_w^4}}$$

$$\text{let } L_w = L_m = L$$

$$\omega_0^2 = \frac{1}{2 C L} + \frac{1}{C L} - \frac{R^2}{2 L^2} \pm \sqrt{\frac{1}{4 C^2 L^2} + \frac{R^2}{2 C L^3} - \frac{R^2}{C L^3} + \frac{R^4}{4 L^4}}$$

$$= \frac{3 L - C R^2}{2 C L^2} \pm \sqrt{\frac{L^2 + 2 R^2 C L - 4 R^2 C L + C^2 R^4}{4 C^2 L^4}}$$

$$= \frac{3 L - C R^2 \pm \sqrt{(L - C R^2)^2}}{2 C L^2}$$


$$= \frac{3 L - C R^2 \pm (L - C R^2)}{2 C L^2}$$

$$\omega_0 = \sqrt{\frac{3 L - C R^2 + L - C R^2}{2 C L^2}} = \sqrt{\frac{4 L - 2 C R^2}{2 C L^2}}$$

$$\omega_0 = \sqrt{\frac{3 L - C R^2 - L + C R^2}{2 C L^2}} = \sqrt{\frac{2 L}{2 C L^2}} = \sqrt{\frac{1}{L C}} \quad (V)$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \rightarrow f_c = \frac{1}{2\pi\sqrt{LC}}$$

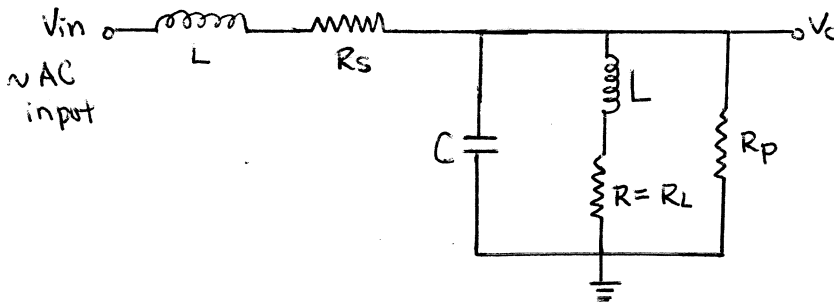Taking component losses and loaded Q into account (@ RF):



R_s = component loss of the matching inductor \rightarrow treat it as a source resistance

R_L = load resistance = $R_w + R_c$

R_p = the true load that the resonant circuit sees \rightarrow equivalent parallel resistance of R_s and R_L

Suppose

$$1) \left. \begin{array}{l} f_c = \text{centre frequency} = 500 \text{ kHz} \\ f_2 - f_1 = 60 \text{ kHz} \end{array} \right\} \text{loaded } Q = \frac{f_c}{f_2 - f_1} = \frac{500 \text{ kHz}}{60 \text{ kHz}} = 8.333$$

$$2) R_s = 1 \text{ k}\Omega \quad \text{where } R_{\text{work}} \text{ and } R_s \text{ should be the same } \therefore L_m = L_w$$

$$\begin{aligned} R_L &= R_w + R_c \\ &= 1 \text{ k} + 500 \\ &= 1.5 \text{ k}\Omega \end{aligned}$$

3) Quality Factor of the inductor: $Q = 85$ (the higher the Q factor is, the closer it approaches the behaviour of an ideal inductor is.)

Soln: Find values of L and C

1) Q factor:

$$Q_p X_p = R_p \rightarrow 85 X_p = R_p \quad (1)$$

2) loaded Q:

$$\text{loaded } Q = \frac{R_{\text{total}}}{X_p} = \frac{R_s // R_L // R_p}{X_p} \quad \text{where } R_s // R_L // R_p = \frac{1000(1500)}{1000+1500} // R_p = 600 // R_p$$

$$= \frac{\frac{600(R_p)}{600+R_p}}{X_p} \quad \text{--- (2)}$$

$$(X_p)8.33 = \frac{600(85X_p)}{600+85X_p}$$

$$5100X_p = X_p(708.05X_p + 4998)$$


$$X_p(708.05X_p - 4602) = 0$$

$$X_p = 64.97 \Omega \quad \text{and} \quad R_p = 5522.45 \Omega$$

$$L = \frac{X_p}{\omega} = \frac{64.97}{2\pi(500 \times 10^3)} = \underline{\underline{20.63 \mu H}}$$

$$C = \frac{1}{\omega X_p} = \frac{1}{2\pi(500 \times 10^3)(64.97)} = \underline{\underline{4.899 \text{ nF}}}$$

Transfer Function and Bode Plot

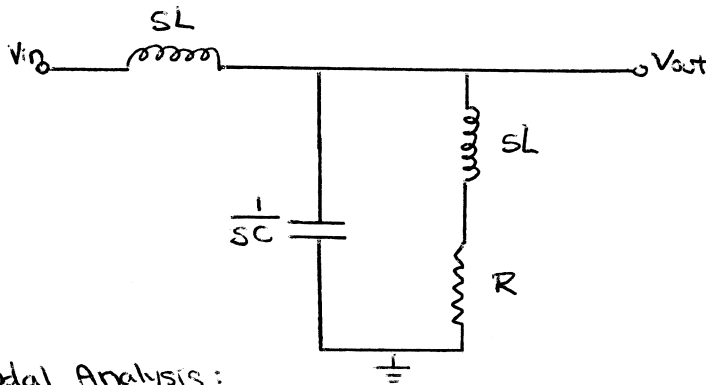

Nodal Analysis:

$$\frac{V_o - V_{in}}{SL} + \frac{V_o}{\frac{1}{sC}} + \frac{V_o}{SL + R} = 0$$

$$V_o \left(\frac{1}{SL} + sC + \frac{1}{SL + R} \right) = \frac{V_{in}}{SL}$$

$$V_o \left(\frac{SL + R + SL + sC \cdot SL(SL + R)}{SL(SL + R)} \right) = \frac{1}{SL} V_{in}$$

$$V_o \left(\frac{2SL + R + sC \cdot (s^2 L^2 + sRL)}{SL(SL + R)} \right) = \frac{1}{SL} V_{in}$$

$$V_o \left(\frac{s^3 CL^2 + s^2 CRL + 2SL + R}{SL(SL + R)} \right) = \frac{1}{SL} V_{in}$$

$$H(s) = \frac{V_o(s)}{V_{in}(s)} = \frac{SL + R}{s^3 CL^2 + s^2 CRL + s(2L) + R}$$

$$= \frac{R(1 + s\frac{L}{R})}{R[s^3(\frac{CL^2}{R}) + s^2(CL) + s(\frac{2L}{R}) + 1]}$$

zero: $s = -R/L$

pdes: $s^3(\frac{CL^2}{R}) + s^2(CL) + s(\frac{2L}{R}) + 1 = 0$

$L = 20.68 \mu H$

$C = 4.899 nF$

$R = 1.5 k\Omega$

MATLAB

$s_1 = -7.2398 \times 10^7 = -7.2398 \times 10^7$

$s_2 = -0.0068 + j0.3144 = -(0.0068 - j0.3144)$

$s_3 = -0.0068 - j0.3144 = -(0.0068 + j0.3144)$

$$H(s) = \frac{1 + s\frac{L}{R}}{(s + \omega_1)(s + \omega_2)(s + \omega_3)} = \frac{1 + s\frac{L}{R}}{\omega_1(1 + \frac{s}{\omega_1})\omega_2(1 + \frac{s}{\omega_2})\omega_3(1 + \frac{s}{\omega_3})}$$

$s = j\omega$

$$H(j\omega) = \frac{1}{\omega_1 \omega_2 \omega_3} \frac{1 + j(\frac{L}{R}\omega)}{(1 + j\frac{\omega}{\omega_1})(1 + j\frac{\omega}{\omega_2})(1 + j\frac{\omega}{\omega_3})}$$

• Phase:

$$\angle H(j\omega) = \angle\left(\frac{1}{\omega_1 \omega_2 \omega_3}\right) + \angle\left(1 + j\frac{\omega}{\omega_R}\right) - \angle\left(1 + j\frac{\omega}{\omega_1}\right) - \angle\left(1 + j\frac{\omega}{\omega_2}\right) - \angle\left(1 + j\frac{\omega}{\omega_3}\right)$$

• Magnitude:

$$20\log_{10}(|H(j\omega)|) = 20\log_{10}\left(\left|\frac{1}{\omega_1 \omega_2 \omega_3}\right|\right) + 20\log_{10}\left(\left|1 + j\frac{\omega}{\omega_R}\right|\right) - 20\log_{10}\left(\left|1 + j\frac{\omega}{\omega_1}\right|\right) - 20\log_{10}\left(\left|1 + j\frac{\omega}{\omega_2}\right|\right) - 20\log_{10}\left(\left|1 + j\frac{\omega}{\omega_3}\right|\right)$$

At this point, please refer to the Bode Plot attached in the email:
 $\omega_r = 3.14 \times 10^6$ rad/s (the peak frequency)

$$f_r = \frac{3.14 \times 10^6 \text{ rad/s}}{2\pi} \approx 500 \text{ kHz}$$

Role of the PLL:

synchronizes frequency of V_{in} (V_{in}) with that of V_c (V_{ost}) so they operate at the same frequency \rightarrow PLL will lock onto the resonant frequency ($f_r = 500 \text{ kHz}$) and maintain a phase difference of 90° between V_c and V_{in} .

the reference
Signal

However, looking at the Phase Plot, at f_r , the ~~of~~ output lags the input signal by 180° ...